

CSE 436/536

Digital Integrated Circuits

Final Project – VLSI Design of Sequential Square Root

Demo Date 14/01/2022 18:00

1. In this assignment, using Magic Layout Tool you will design a 0.25um TSMC process standard cell for D flip flop.
2. Design a sequential circuit that can find square root of a number N. N is a 8-bit number.

Your circuit will try all integers until half of N. When the resultant square becomes higher than N it selects the last number as the result.

For instance let's assume N is 53, then your circuit tries all numbers from 1 to $53/2 = 26$. When it tries 8, the result is 64 which is greater than 53 so the result is 7.

- ✓ First draw the state diagram. Try to draw the simplest diagram for that. Because it eases your design.
- ✓ Then draw the state table and draw the schematic of your design on Logisim. Make sure it works in Logisim.
- ✓ Draw your layout on Magic tool using the standard cells you designed. You have to use hierarchy.
- ✓ Convert your design to Spice and show the functional accuracy of your design and the delay of your circuit for N = 255.
- ✓ Put your State Diagram, State Table, Logisim circuit, Magic layouts, your Spice extracted circuit deck and Spice results into a zip file. Name your zip file as:

StudentName_StudentSurname_StudentId_FinalProject.zip