

**CSE 436/536**

**Digital Integrated Circuits**


**Final Project -VLSI Design of Sequential Square Root**

**1801042103**


**Ozan GEÇKİN**

 
1. In this assignment, using Magic Layout Tool you will design a 0.25um TSMC process standard cell for D flip flop.

First, I made the drawing with the gates.



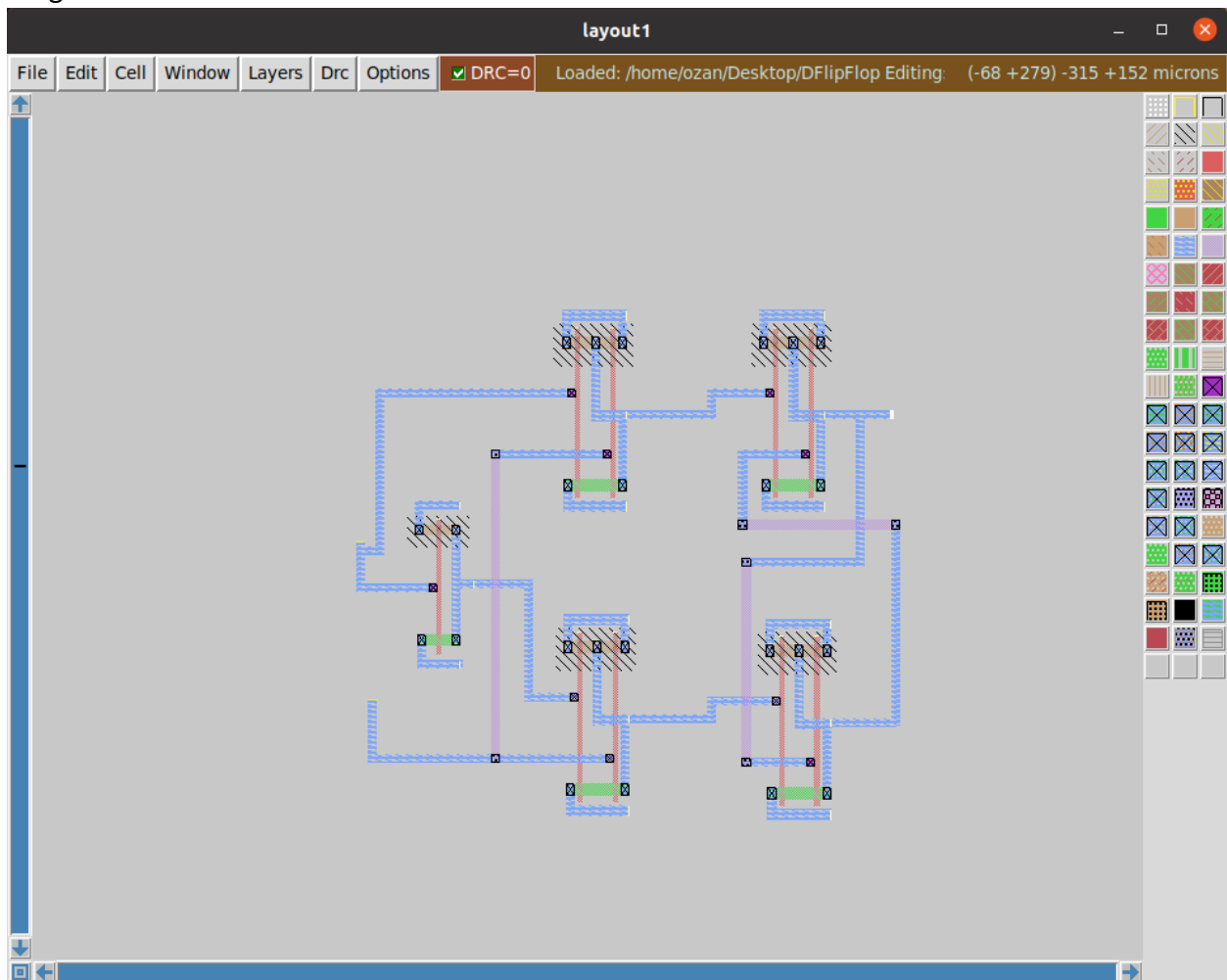Then I completed my drawing in magic with 4 NAND2 and 1 inverter by making hierarchy with Magic cell.



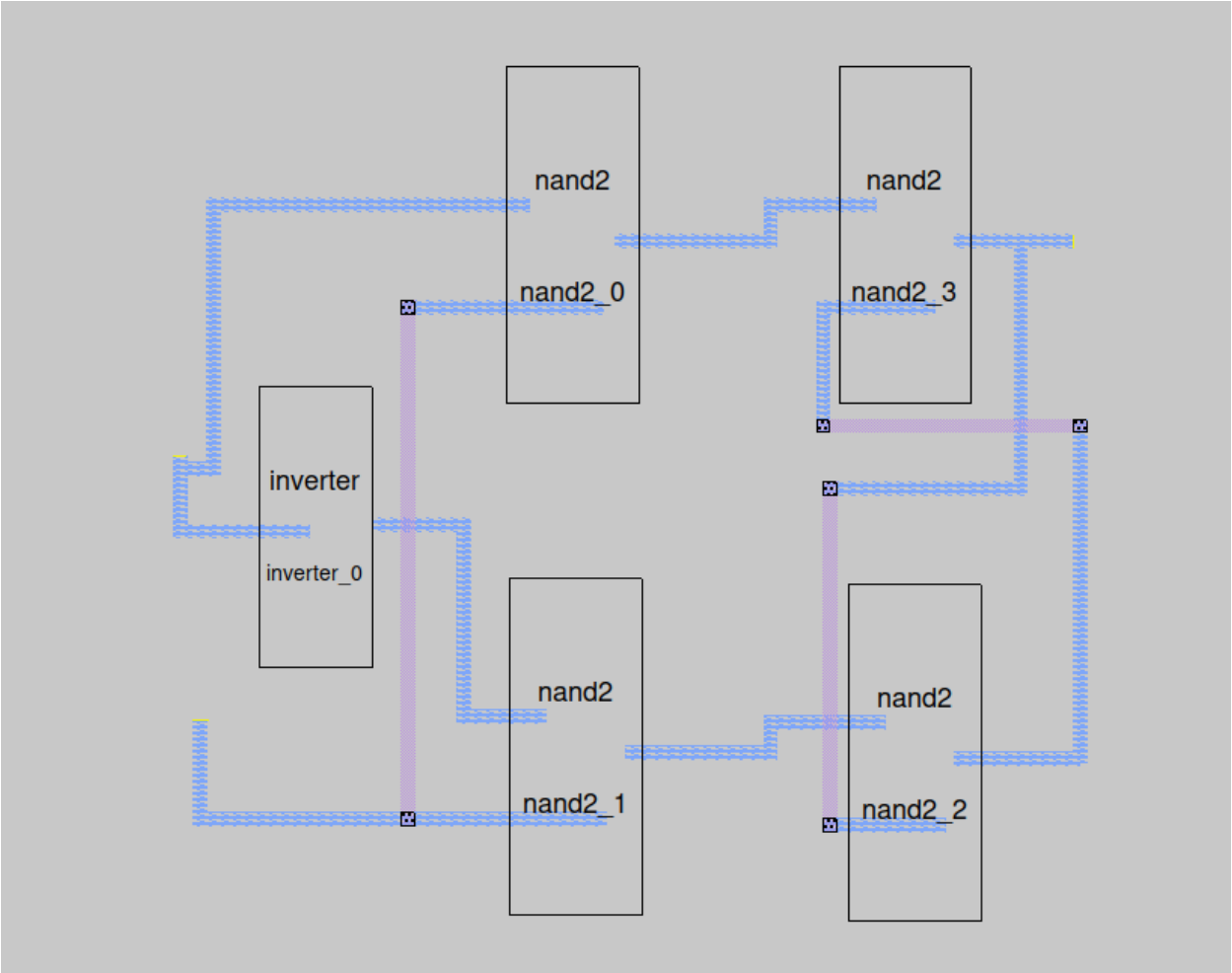

For Question 2, I could only draw a state diagram.

